


Module 5 :- Sequential design

Topics

Introduction, Mealy and Moore models, State machine notation, synchronous sequential circuit analysis and design.

Sequential design.

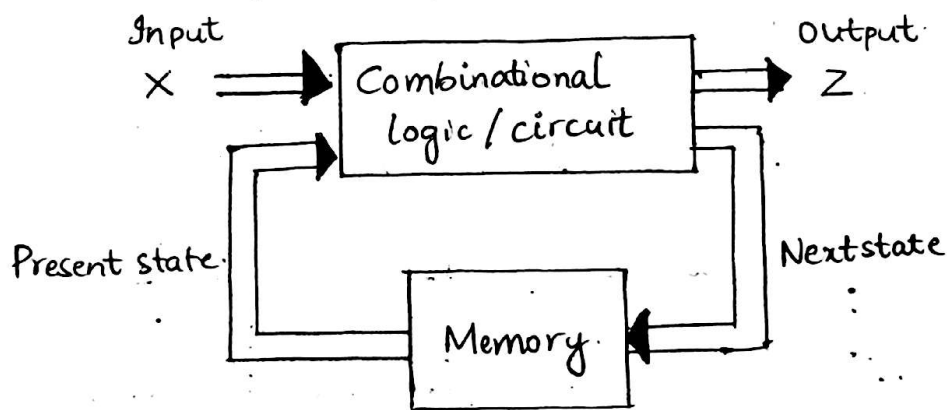- Includes systematic analysis of simple sequential machine.
- The clocked synchronous sequential circuits have master clock which is connected simultaneously to the controlled clock input of all the flip flops in the memory block of the circuit.
- The figure below shows the general configuration of a clocked synchronous sequential circuit input.




There are two sequential models called.

1) Mealy model.

2) Moore model.

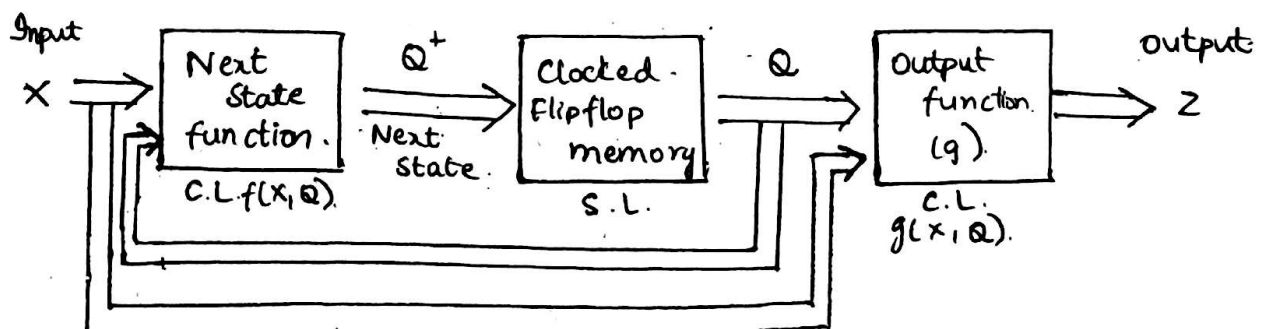1) Mealy model.

C.L - combinational logic
S.L - sequential logic.




If X denoted the collective external input signal and Q the collective present state of the flipflop then the next state of the network denoted by -
 $Q^+ = f(X, Q)$.


similarly. if Z is regarded as the collective output signals of the network then under the assumption that the output are the function of both input and present state.

$$Z = g(X, Q)$$

② Moore model.

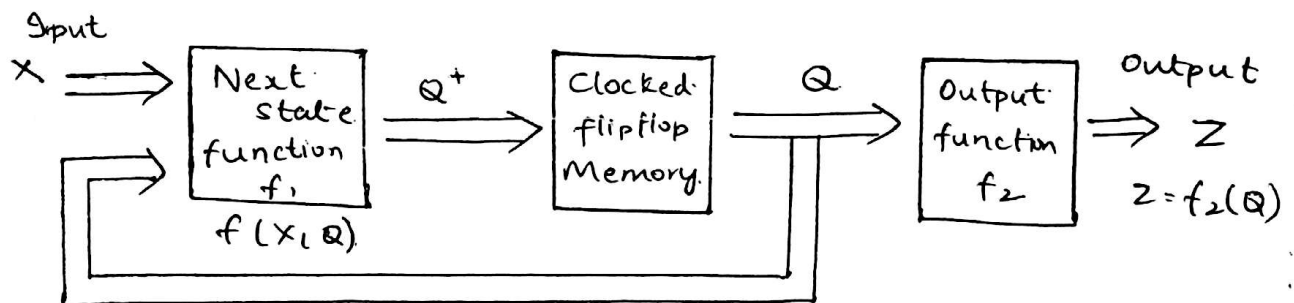

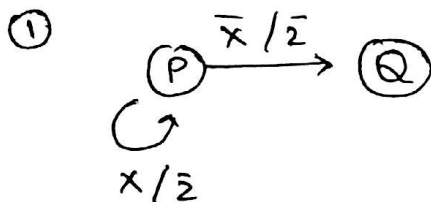I identify the type of machine [Mealy / Moore]



$$Q^+ = f(X, Q)$$

$$Z = f(X, Q)$$

$X \rightarrow$ input

$Z \rightarrow$ output

Numerator \rightarrow Input

Denominator \rightarrow output

$Q \rightarrow$ present state

$Q^+ \rightarrow$ Next state.

Mealy model.

- There are two states 'P' and 'Q'

- When at state P

\rightarrow If the input is 1, it remains at state P and output is zero


→ If the input is '0', it makes a transition to the state Q and the output is '0'. Therefore transition to the state Q and the output is '0'. Therefore

$$Q^+ = f(x, Q)$$

$$Z = f(x, Q)$$

This is a mealy model.

(2)

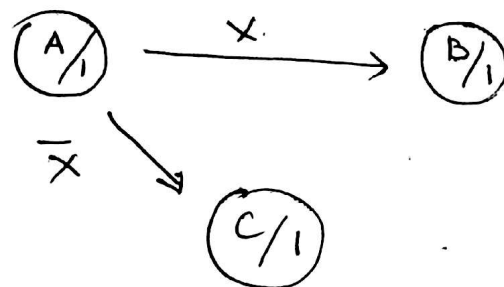

$$Q^+ = f(x, Q)$$

$$Z = f(Q)$$

Moore model.


Analysis of sequential circuits.

- Combinational circuits are easy to analyse, we need to write boolean expression for the outputs and write the truth table.
- The operation of sequential circuit is not quite apparent from the diagram
- We need to write the state diagram in order to understand the sequence of state for every clock pulse applied.

The procedure to analyse synchronous circuit is as follows:-

- Identify the state variables. [Flip flop o/p]
- Identify the flip flop type.
- Write the flipflop input equations.
- Construct K-map using flip flop equation.
- Write the state diagram from state transition table.

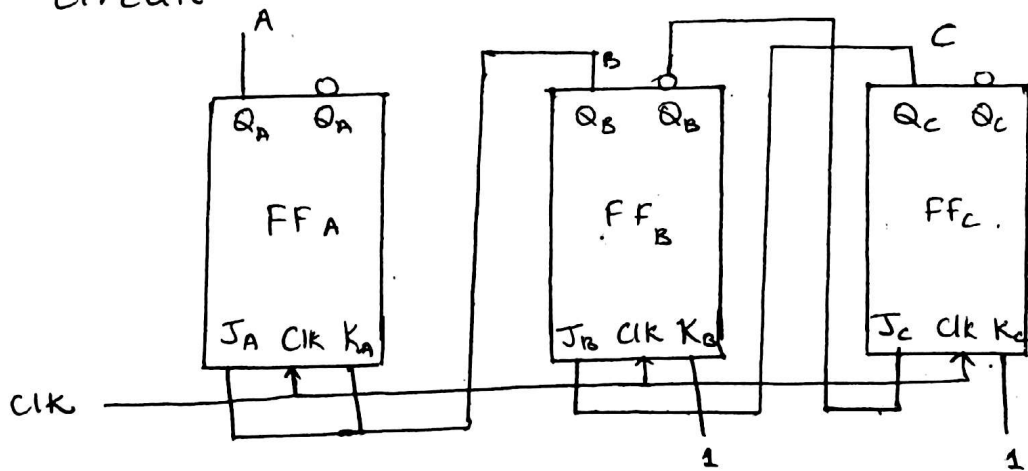Analyse the following synchronous sequential circuit.



Soln ① There are 3 state variable
A, B, C.

② All are JK flip flop.

③ $J_A = Q_B$, $K_A = \overline{Q_B}$

$J_B = Q_C$, $K_B = 1$

$J_C = \overline{Q_B}$, $K_C = 1$.

④ K-map.

J_A & K_A

$Q_A Q_B$	00	01	11	10
0	0	1	1	0
1	0	1	1	0

J_B

$Q_A Q_B$	00	01	11	10
0	0	0	0	0
1	1	1	1	1

$K_B \& K_C$

$Q_A Q_B$	00	01	11	10
$Q_C = 0$	1 ₀	1 ₂	1 ₆	1 ₄
$Q_C = 1$	1 ₁	1 ₃	1 ₇	1 ₅

J_C


$Q_A Q_B$	00	01	11	10
$Q_C = 0$	1 ₀	0 ₂	0 ₆	1 ₄
$Q_C = 1$	1 ₁	0 ₃	0 ₇	1 ₅

State transition table.


Decided from P.S & JK

P.S			N.S								
Q_A	Q_B	Q_C	Q_A^+	Q_B^+	Q_C^+	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	0	1	0	0	0	1	1	1
0	0	1	0	1	0	0	0	1	1	1	1
0	1	0	1	0	0	1	1	0	1	0	1
0	1	1	1	0	0	1	1	1	1	0	1
1	0	0	1	0	1	0	0	0	1	1	1
1	0	1	1	1	0	0	0	1	1	1	1
1	1	0	0	0	0	1	1	0	1	0	1
1	1	1	0	0	0	1	1	1	1	0	1

State diagram

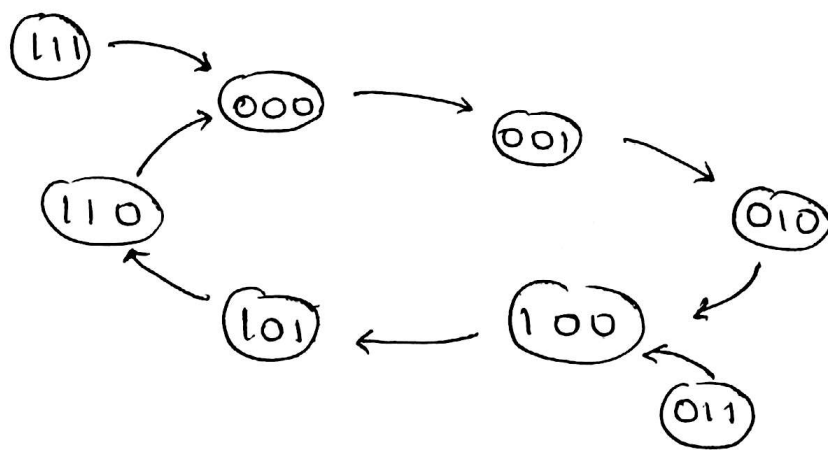

Analyze synchronous sequential circuit:

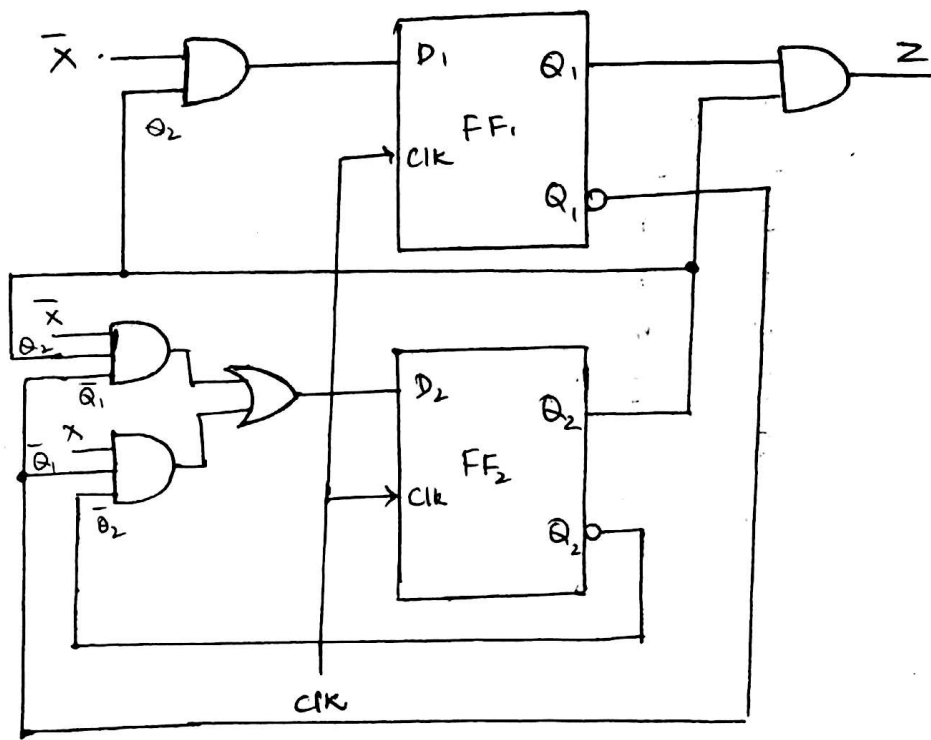

Soln ① There are 2 state variable

 Q_1, Q_2

② Both are D flip flop

(3) $D_1 = Q_2 \overline{x}$

$$\begin{aligned} D_2 &= \bar{x} \odot_2 \bar{Q}_1 + \bar{Q}_1 \odot_2 x \\ &= \bar{Q}_1 (\bar{x} \odot_2 + \bar{Q}_2 x) \\ &= \bar{Q}_1 (Q_2 \oplus x) \end{aligned}$$

$$Z = Q_2 Q_1 = Q_1 Q_2$$

K-map.

D_1

$Q_1 Q_2$	00	01	11	10
0	0	1	1	0
1	0	0	0	0

D_2

	$Q_1 Q_2$	00	01	11	10
x	0	0	1 ₂	0 ₆	0 ₄
1	1	1 ₁	0 ₃	0 ₇	0 ₅

Q_1, Q_2


Z

X	00	01	11	10
0	0	0	1	0
1	0	0	1	0


State transition.

P.S			N-S		D ₁	D ₂	Z
Q ₁	Q ₂	X	Q ₁ ⁺	Q ₂ ⁺			
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	1	1	1	1	0
0	1	1	0	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0
1	1	0	1	0	1	0	1
1	1	1	0	0	0	0	1

Moore model.

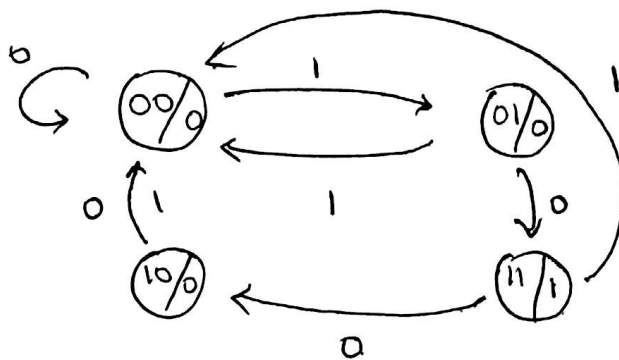

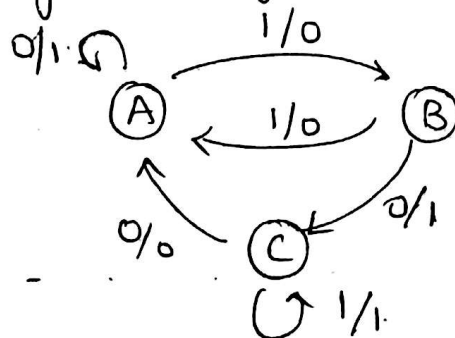Realise the system represented by the following State diagram using D-FF



Soln

In order to generate 3 states, we require 2 flipflops.

State assignment.

Assuming $A = 00$
 $B = 01$
 $a = 10$

P.S			N.S		D_1	D_2	Z
Q_1	Q_2	X	Q_1^+	Q_2^+			
0	0	0	0	0	0	0	1
0	0	1	0	1	0	1	0
0	1	0	1	0	1	0	1
0	1	1	0	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	0	1	0	1
1	1	0	X	X	X	X	X
1	1	1	X	X	X	X	X

K-map

D_1

Q_1, Q_2	00	01	11	10
X=0	0 ₀	1 ₂	X ₆	0 ₄
X=1	0 ₁	0 ₃	X ₇	1 ₅

$$D_1 = Q_2 \bar{X} + Q_1 X$$

D_2

Q_1, Q_2	00	01	11	10
X=0	0 ₀	0 ₂	X ₆	0 ₄
X=1	1 ₁	0 ₃	X ₇	0 ₅


$$D_2 = \bar{Q}_1 \bar{Q}_2 X$$

Z


Q_1, Q_2	00	01	11	10
X=0	1 ₀	1 ₂	X ₆	0 ₄
X=1	0 ₁	0 ₃	X ₇	1 ₅

$$Z = \bar{Q}_1 \bar{X} + Q_1 X$$

$$= \bar{Q}_1 \oplus X$$

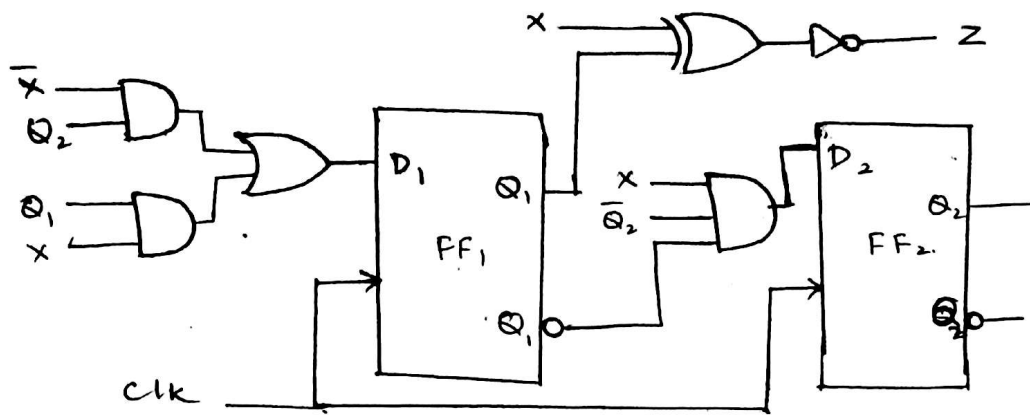

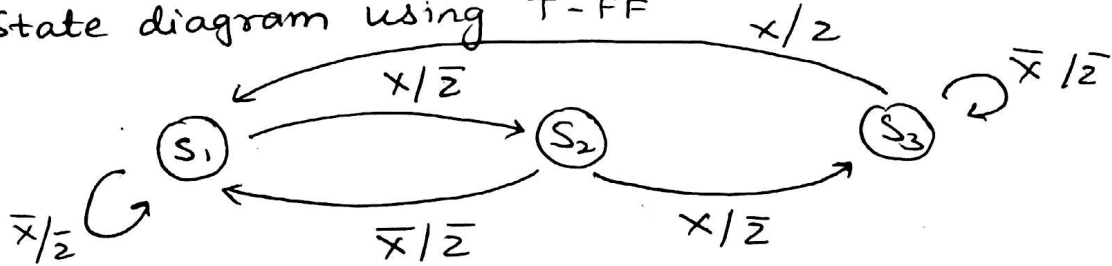Realise the System represented by the following State diagram using T-FF







Soln we use 2 flip flops for 3 states.

Assume $S_1 = 00$
 $S_2 = 01$
 $S_3 = 10$


P.S.			N.S.		T_1	T_2	Z
Q_1	Q_2	X	Q_1^+	Q_2^+			
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	0	0	1	0
0	1	1	1	0	1	1	0
1	0	0	1	0	0	0	0
1	0	1	0	0	1	0	1

K-map.

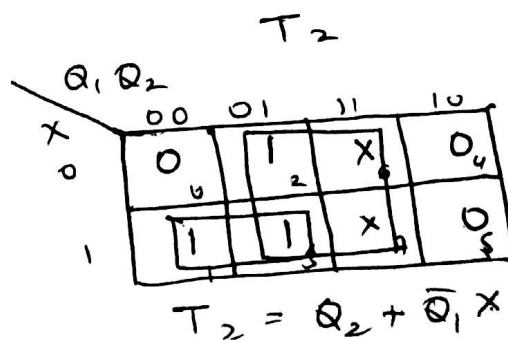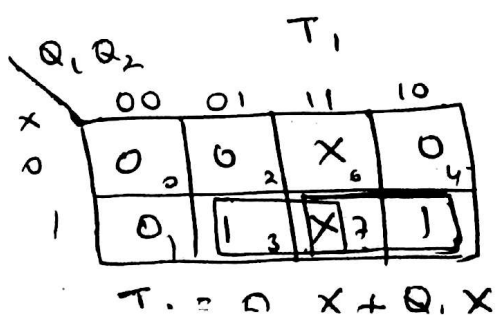

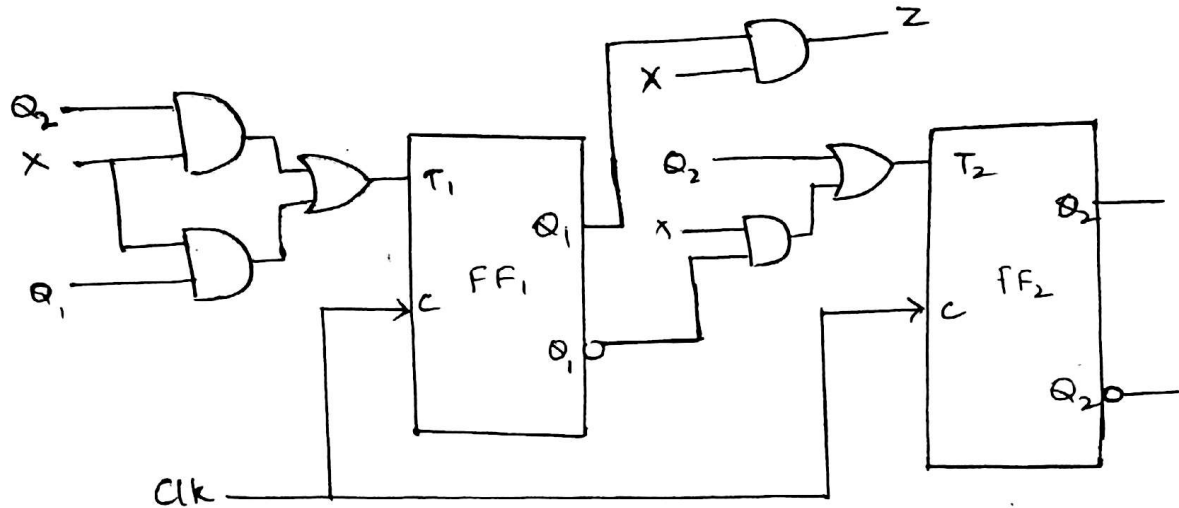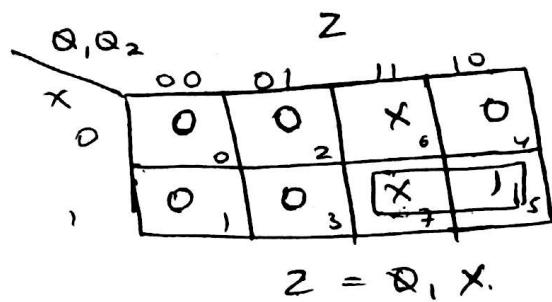

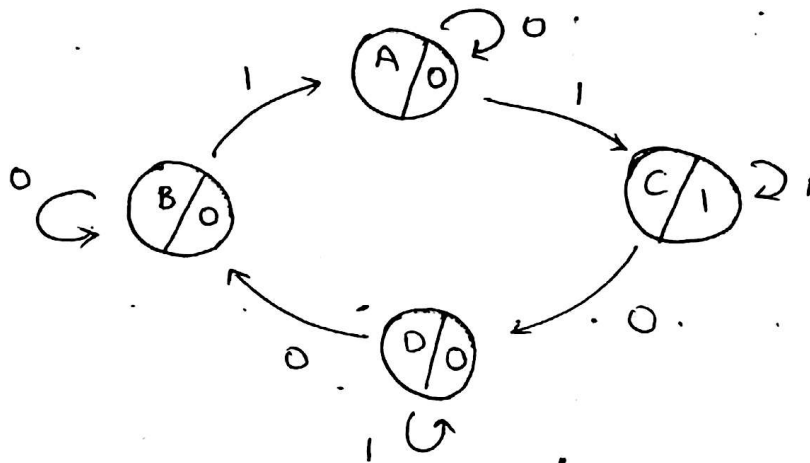Realise the circuit diagram using JK flip flop



Soln We use 2 flip flops for 4 states.

Assume :-

$$A = 00$$

$$B = 01$$

$$C = 10$$

$$D = 11$$

P.S			N.S.		$J_1 K_1$		$J_2 K_2$		Z
Q_1	Q_2	X	Q_1^+	Q_2^+					
0	0	0	0	0	0	X	0	X	0
0	0	1	1	0	1	X	0	X	0
0	1	0	0	1	0	X	X	0	0
0	1	1	0	0	0	X	X	1	0
1	0	0	1	1	X	0	1	X	1
1	0	1	1	0	X	0	0	X	1
1	1	0	0	1	X	1	X	0	0
1	1	1	1	1	X	0	X	0	0

Kmap

J_1

Q_1, Q_2	00	01	11	10
X=0	0 ₀	0 ₂	X ₆	X ₄
X=1	1 ₁	0 ₃	X ₇	X ₅

$J_1 = \overline{Q_2} X$

K_1

Q_1, Q_2	00	01	11	10
X=0	X ₀	X ₂	1 ₆	0 ₄
X=1	X ₁	X ₃	0 ₇	0 ₅

$K_1 = Q_2 \overline{X}$

J_2

Q_1, Q_2	00	01	11	10
X=0	0 ₀	X ₂	X ₆	1 ₄
X=1	0 ₁	X ₃	X ₇	0 ₅

$J_2 = Q_1 \overline{X}$

K_2


Q_1, Q_2	00	01	11	10
X=0	X ₀	0 ₂	0 ₆	X ₄
X=1	X ₁	1 ₃	0 ₇	X ₅

$K_2 = \overline{Q_1} X$


Z

Q_1, Q_2	00	01	11	10
X=0	0 ₀	0 ₂	0 ₆	1 ₄
X=1	0 ₁	0 ₃	0 ₇	1 ₅

$Z = Q_1 \overline{Q_2}$

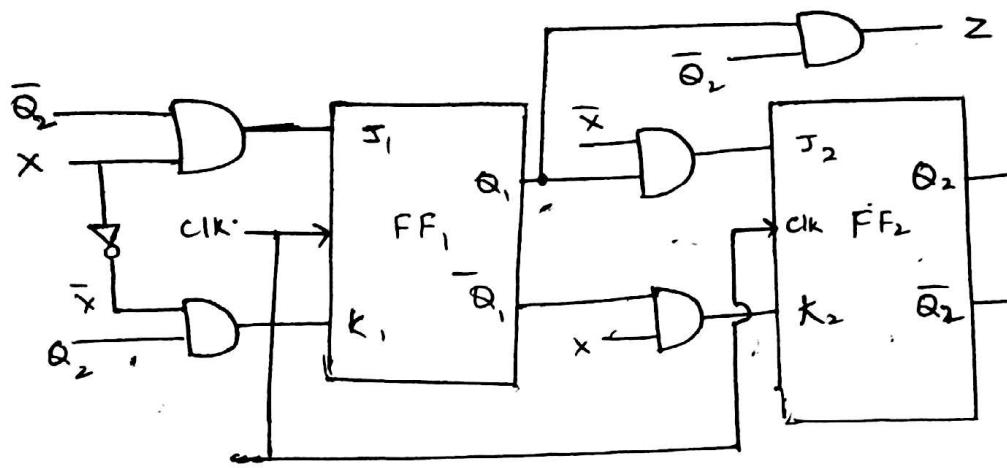

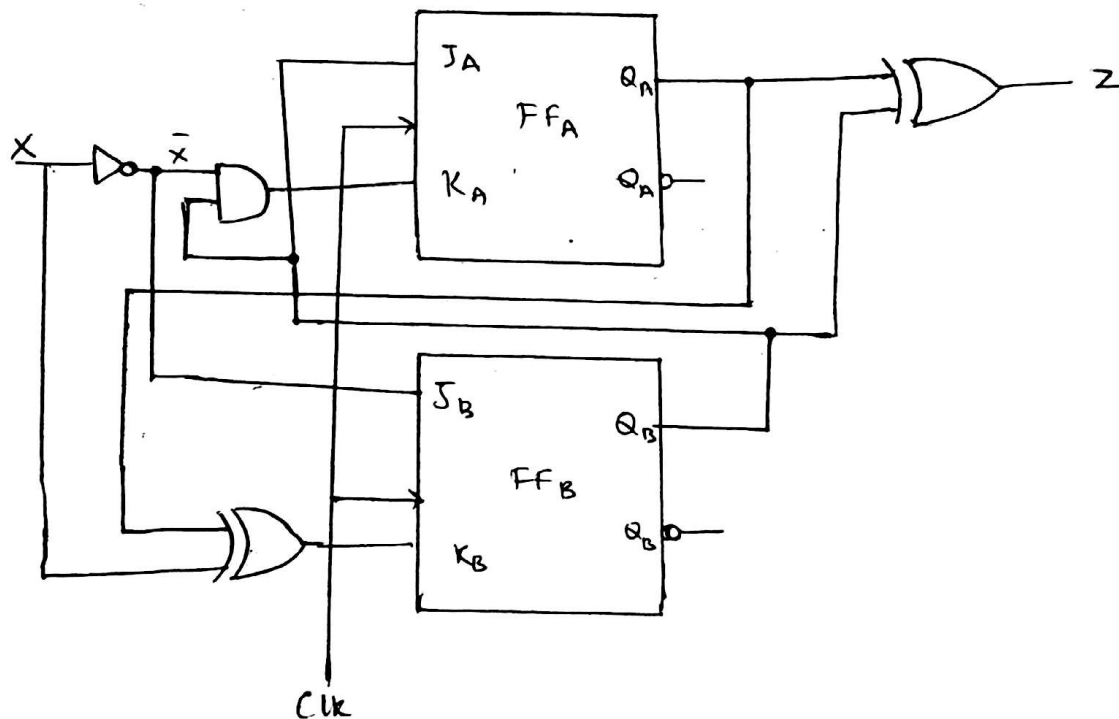Analysar synchronous sequential circuit -



Soln ^{have} we used 2 flipflop.
All are J K flipflops.

$$J_A = Q_B$$






$$K_A = \bar{X} Q_B$$

$$J_B = \bar{X}$$

$$K_B = Q_A \bar{X} + X \bar{Q}_A$$

$$Z = Q_B \bar{Q}_A + Q_A \bar{Q}_B$$

K-map

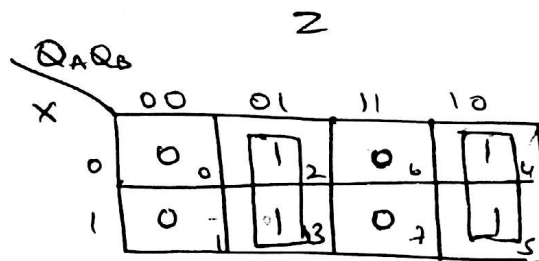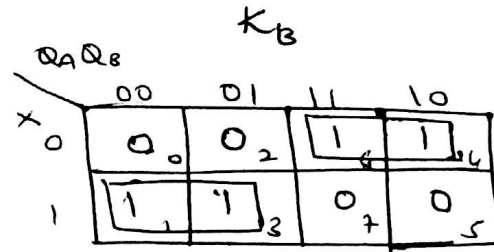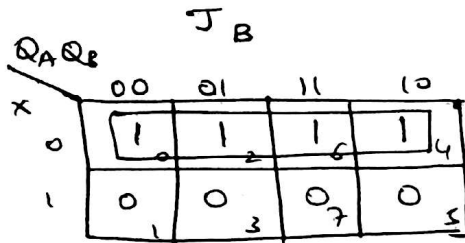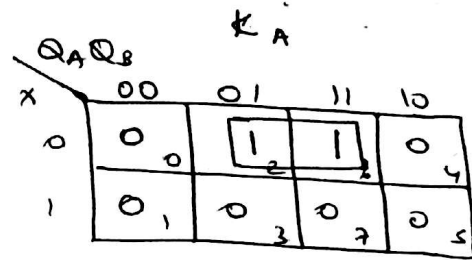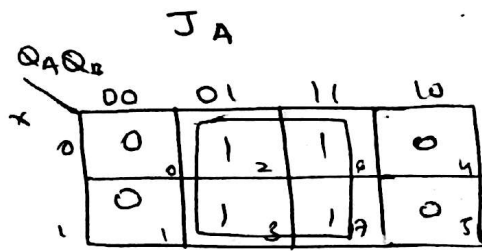

P.S.			N.S.		$J_A \quad K_A$		$J_B \quad K_B$		Z
Q_A	Q_B	X	Q_A^+	Q_B^+					
0	0	0	0	1	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0
0	1	0	1	1	1	1	1	0	1
0	1	1	1	0	1	0	0	1	1
1	0	0	1	0	0	0	1	1	1
1	0	1	1	1	0	0	0	0	1
1	1	0	0	0	1	1	1	1	0
1	1	1	1	1	1	0	0	0	0

