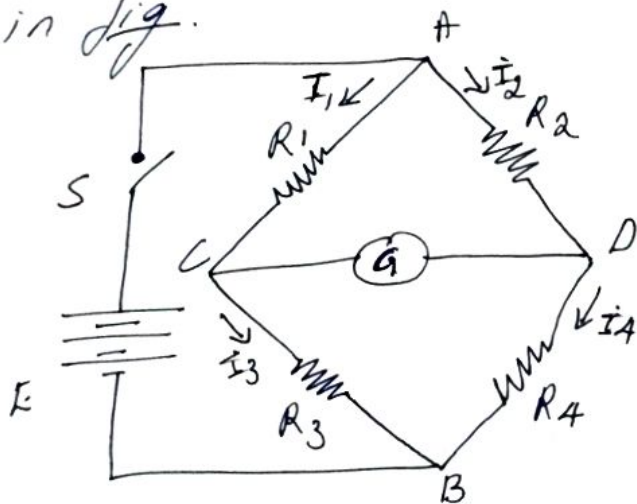


## UNIT - 1.

### Measurement of resistance, Inductance & Capacitance.

#### Introduction

A bridge circuit in its simplest form consists of a network of four resistance arms forming a closed circuit, with a dc source of current applied to two opposite junctions and a current detector connected to the other two junctions as shown in fig.



Bridge circuits are extensively used for measuring component values such as  $R$ ,  $L$  &  $C$ . Since the bridge circuit merely compares the value of an unknown component with that of an accurately known component (a standard), its measurement accuracy can be high.

The basic dc bridge is used for accurate measurement of resistance & is called wheatstone's bridge.

wheatstone's bridge (measurement of Resistance).

This is the most accurate method for measuring resistances. The ckt diagram is as in fig above. The source of emf & switch is connected to points A & B, while a sensitive current indicating meter, the galvanometer is connected to points C & D.

The galvanometer is a microammeter, with a zero centre scale. When there is no current thro' the meter, the galvanometer pointer rests at 0, i.e. mid scale. Current in one direction causes the pointer to deflect on one side & current in the opposite direction to the other side.

When 'S' is closed, current flows & divides into the two arms at point A i.e.  $i_1$  &  $i_2$ . The bridge is balanced when there is not current thro' the galvanometer or when the potential difference at points C & D is equal.

To obtain bridge balance.

2

$$I_1 R_1 = I_2 R_2 \rightarrow (1)$$

for the galvanometer current to be zero. The following conditions should be satisfied

$$I_1 = I_3 = \frac{E}{R_1 + R_3} \rightarrow (2)$$

$$I_2 = I_4 = \frac{E}{R_2 + R_4} \rightarrow (3)$$

Sub (2) & (3) in (1)

$$\frac{E}{R_1 + R_3} \cdot R_1 = \frac{E}{R_2 + R_4} \cdot R_2$$

$$R_1(R_2 + R_4) = R_2(R_1 + R_3)$$

$$R_1 R_2 + R_1 R_4 = R_1 R_2 + R_2 R_3$$

$$R_1 R_4 = R_2 R_3$$

$$R_4 = \frac{R_2 R_3}{R_1}$$

This is the equation for the bridge to be balanced.

$R_4$  can be considered as unknown resistance  $R_x$ .

Eg:- Fig @ consists of the following parameters

$R_1 = 10K$ ,  $R_2 = 15K$ ,  $R_3 = 40K$ . Find the unknown resistance

$R_x$ .

$$\text{w.k.T } R_x = \frac{R_2 R_3}{R_1} = \frac{15K \times 40K}{10K} = \underline{\underline{60K\Omega}}$$




## Limitations

- 1] For low resistance measurement, the resistance of the leads and contacts becomes significant & introduces error (eliminated by Kelvin's Bridge)
- 2] For high resistance measurements, the resistance presented by bridge becomes so large that the galvanometer is insensitive to imbalance. Therefore for high resistance measurements wheatstone's bridge cannot be used.
- 3] When current flows through the resistance due to heating effect there is change in resistance of the bridge arms
- 4] Excessive current may cause a permanent change in value.
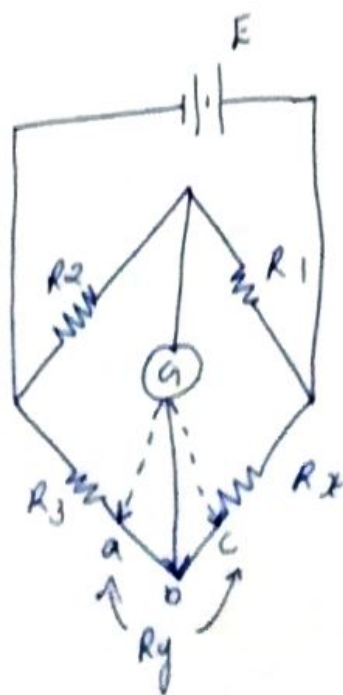
## Kelvin's Bridge

Kelvin's Bridge is a modification of wheatstone's bridge and is used to measure values of resistance below  $1\Omega$



3

In low resistance measurement, the resistance of the leads connecting the unknown resistance to the terminal of the bridge circuit may affect the measurement.

Let  $R_y$  = resistance of the connecting leads from  $R_3$  to  $R_x$

The galvanometer can be connected either to point 'c' or to point 'a'. When it is connected to point a, the resistance  $R_y$  of the connecting lead is added to the unknown resistance  $R_x$ .

When the connection is made to point 'c',  $R_y$  is added to the bridge arm  $R_3$  & the resulting measurement of  $R_x$  is lower than the actual value, because now the actual value of  $R_3$  is higher than its nominal value by the resistance  $R_y$ .

If it is connected to point b, in such a way that the ratio of the resistance from c to b & that from a to b equal the ratio of resistances  $R_1$  &  $R_2$  then.

$$\text{And } \frac{R_{cb}}{R_{ab}} = \frac{R_1}{R_2} \rightarrow \textcircled{1}$$

W.K.T balance eqn is

$$R_1 R_3 = R_2 R_x$$

applying this to the above bridge.

$$R_1 (R_3 + R_{ab}) = R_2 (R_x + R_{cb}).$$

$$(R_3 + R_{ab}) \frac{R_1}{R_2} = R_x + R_{cb} \rightarrow \textcircled{2}$$

but from ① W.K.T  $\frac{R_1}{R_2} = \frac{R_{cb}}{R_{ab}}$

$$\& R_{ab} + R_{cb} = R_y \rightarrow \textcircled{3}$$

$$\text{W.K.T } \frac{R_1}{R_2} = \frac{R_{cb}}{R_{ab}}$$

adding 1 to both sides

$$\frac{R_{cb}}{R_{ab}} + 1 = \frac{R_1}{R_2} + 1$$

$$\frac{R_{cb} + R_{ab}}{R_{ab}} = \frac{R_1 + R_2}{R_2}$$

from ③

$$\frac{R_y}{R_{ab}} = \frac{R_1 + R_2}{R_2}$$

$$\therefore R_{ab} = \frac{R_2 R_y}{R_1 + R_2} \rightarrow \textcircled{4}$$



from (3) w.k.T

$$R_{ab} + R_{cb} = R_y.$$

$$R_{cb} = R_y - R_{ab}.$$

Sub (4).

$$R_{cb} = R_y - \frac{R_2 R_y}{R_1 + R_2}$$

$$\therefore R_{cb} = \frac{R_1 R_y + R_2 R_y - R_2 R_y}{R_1 + R_2}.$$

$$\underline{\underline{R_{cb} = \frac{R_1 R_y}{R_1 + R_2} \quad \text{--- (5)}}}$$

Sub (4) & (5) in (2).

$$R_x + \frac{R_1 R_y}{R_1 + R_2} = \left( R_3 + \frac{R_2 R_y}{R_1 + R_2} \right) \frac{R_1}{R_2}.$$

$$R_x + \frac{R_1 R_y}{R_1 + R_2} = \frac{R_1 R_3}{R_2} + \frac{R_1 R_y}{R_1 + R_2}.$$


$$\therefore \underline{\underline{R_x = \frac{R_1 R_3}{R_2} \quad \text{--- (A)}}}$$

This is the usual wheatstone's balance eqn  
 $\propto$  it indicates that the effect of the resistance  
 of the connecting leads from ont a to ont c has

been eliminated by connecting the galvanometer to an intermediate position b.
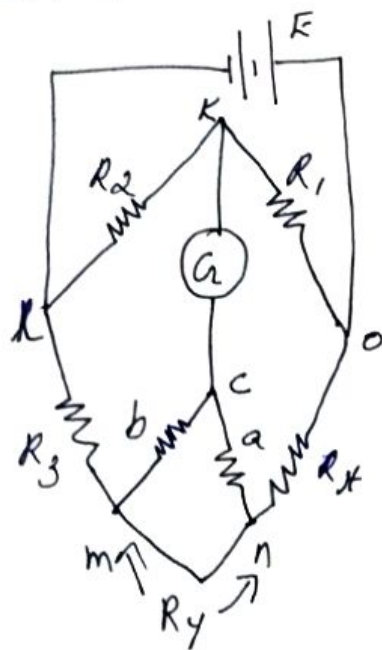
### Kelvin's Double Bridge.

It is called double bridge because it incorporates a second set of ratio arms.




The second set of arms a & b, connect the galvanometer to point 'c' at the appropriate potential between m & n. connection i.e  $R_y$ .

The ratio of the resistances of arms a & b is the same as the ratio of  $R_1$  &  $R_2$ . The galvanometer indication is zero when the potentials at K & c are equal.

$$\therefore E_{KX} = E_{Lmc}$$




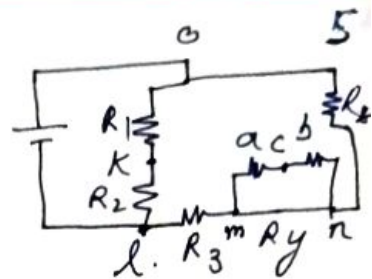But  $E_{LK} = \frac{E \cdot R_2}{R_1 + R_2} \quad \text{--- (1)}$



&  $E = I(R_x + R_3 + (a+b) \parallel R_y) \quad \text{--- (2)}$

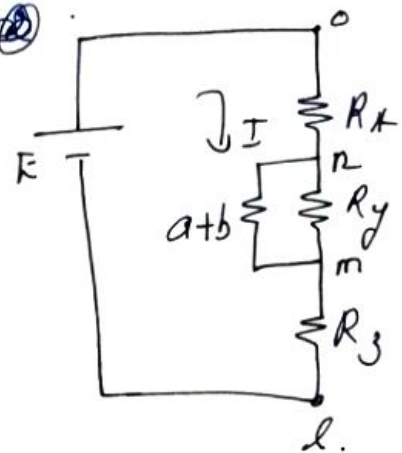$\therefore E = I \left( R_x + R_3 + \frac{(a+b)R_y}{a+b+R_y} \right) \quad \text{--- (2)}$



Sub (2) in (1)


$E_{LK} = \frac{R_2}{R_1 + R_2} \cdot \left[ I \left( R_x + R_3 + \frac{(a+b)R_y}{a+b+R_y} \right) \right] \rightarrow \text{--- (A)}$

|||/y

$E_{lm} = I \cdot R_3 + E_{mc} \rightarrow \text{--- (3)}$

$E_{mc} = \frac{E_{mn} \cdot b}{a+b} \quad \text{--- (4)}$

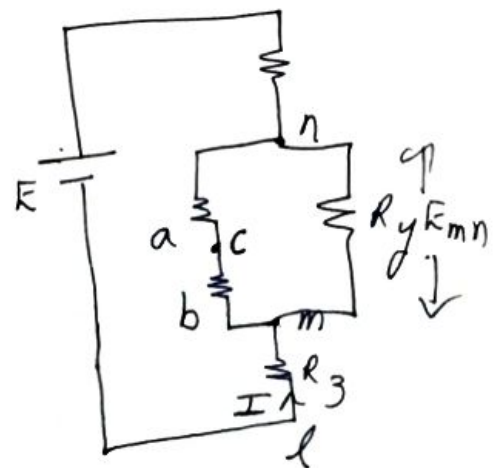&  $E_{mn} = I \cdot R_y \parallel (a+b)$   
 $= I \left[ \frac{(a+b) \cdot R_y}{a+b+R_y} \right] \quad \text{--- (5)}$



$E_{lm} = E_{lm} + E_{mc}$   
 $= I \cdot R_3 + E_{mc}$

Sub (5) in (4)

$E_{mc} = I \left[ \frac{(a+b)R_y}{a+b+R_y} \right] \cdot \frac{b}{a+b} \rightarrow \text{--- (6)}$

Sub (6) in (3)

$$E_{lmc} = \cancel{E_0} I R_3 + I \frac{b}{a+b} \left[ \frac{(a+b) R_y}{a+b+R_y} \right]$$

$$E_{lmc} = I \left[ R_3 + \frac{b}{a+b} \left[ \frac{(a+b) R_y}{a+b+R_y} \right] \right] \rightarrow (B)$$

But  $E_{lk} = E_{lmc}$

using (A) & (B)

$$\frac{I R_2}{R_1 + R_2} \left[ R_3 + R_x + \frac{(a+b) R_y}{a+b+R_y} \right] = I \left[ R_3 + \frac{b}{a+b} \left[ \frac{(a+b) R_y}{a+b+R_y} \right] \right]$$

$$R_3 + R_x + \frac{(a+b) R_y}{a+b+R_y} = \frac{R_1 + R_2}{R_2} \left[ R_3 + \frac{b R_y}{a+b+R_y} \right]$$

$$R_3 + R_x + \frac{(a+b) R_y}{a+b+R_y} = \frac{R_1 R_3}{R_2} + R_3 + \frac{b R_1 R_y}{(a+b+R_y) R_2} + \frac{b R_y}{a+b+R_y}$$

$$R_x = \frac{R_1 R_3}{R_2} + \frac{b R_1 R_y}{(a+b+R_y) R_2} + \frac{b R_y}{a+b+R_y} - \frac{(a+b) R_y}{a+b+R_y}$$

$$= \frac{R_1 R_3}{R_2} + \frac{b R_1 R_y}{R_2 [a+b+R_y]} + \frac{b R_y - a R_y - b R_y}{a+b+R_y}$$

$$= \frac{R_1 R_3}{R_2} + \frac{b R_1 R_y}{R_2 [a+b+R_y]} - \frac{a R_y}{a+b+R_y}$$

$$R_x = \frac{R_1 R_3}{R_2} + \frac{b R_y}{a+b+R_y} \left[ \frac{R_1}{R_2} - \frac{a}{b} \right]$$

but w.k.T  $\frac{R_1}{R_2} = \frac{a}{b}$

$$\therefore \underline{R_x = \frac{R_1 R_3}{R_2}}$$


It indicates that the resistance of the connecting lead  $R_y$ , has no effect on the measurement provided that the ratios of resistance of the two sets of ratio arms are equal

In this bridge the range of resistance covered is  $1 - 0.00001 \Omega$  ( $10 \mu\Omega$ ) with accuracy of  $\pm 0.05\%$  to  $\pm 0.2\%$ .

Eg. If in fig below the ratio of  $R_a$  to  $R_b$  is  $1000 \Omega$ ,  $R_1 = 5 \Omega$  &  $R_1 = 0.5 R_2$ . What is the value of  $R_x$

w.k.T  $R_x = \frac{R_2 R_3}{R_1} \rightarrow \textcircled{1}$

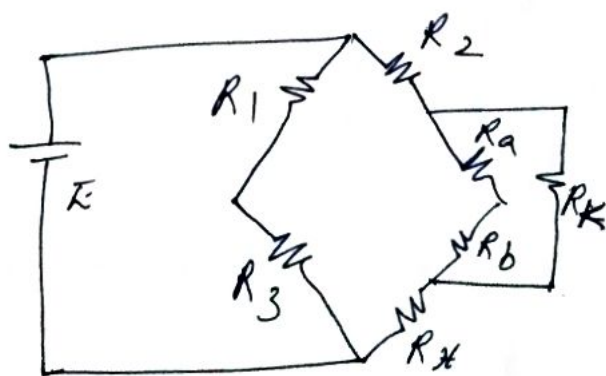8.  $\frac{R_1}{R_3} = \frac{R_a}{R_b} = 1000$





$$\therefore \frac{R_3}{R_1} = \frac{R_b}{R_a} = \frac{1}{1000} \rightarrow (2)$$

$$R_2 = \frac{R_1}{0.5}$$

$$= \frac{5}{0.5} \rightarrow (3)$$

$$R_x = R_2 \left( \frac{R_3}{R_1} \right)$$

$$= \frac{5}{0.5} \left( \frac{1}{1000} \right)$$

$$= \underline{\underline{0.01 \Omega}}$$


### AC Bridges

Impedance at audio & radio freq is commonly determined by means of a.c bridges.

The a.c bridge in their basic form consists of four arms, an a.c source & a null detector i.e. Galvanometer is replaced by detector such as a pair of headphones for detecting a.c

When the bridge is balanced


$$\frac{Z_1}{Z_3} = \frac{Z_2}{Z_4}$$

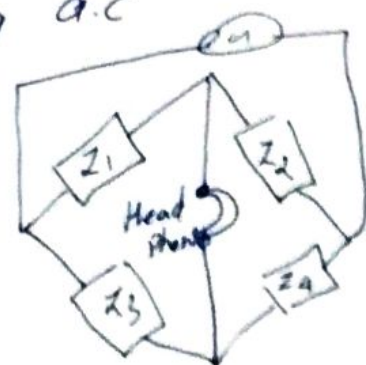

where  $Z_1, Z_2, Z_3$  &  $Z_4$  are the impedances of the arms and are vector complex quantities that possess phase angles.  $\therefore$  it is necessary to adjust both the magnitude & phase angles of the impedance arms to achieve balance i.e. the bridge must be balanced for both the reactance and the resistive component. The phase angles are +ve for inductive impedances & -ve for capacitive impedance.  $(R - jX_C)$   $X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$

Capacitance Comparison Bridge

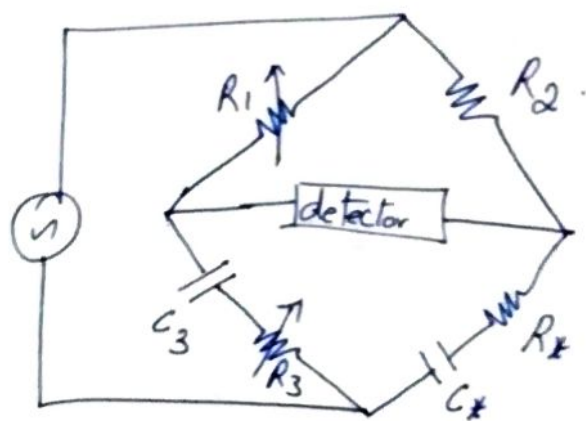The ratio arms  $R_1, R_2$  are resistive. The known standard capacitor  $C_3$  is in series with  $R_3$ .



$R_3$  may also include an added variable resistance needed to balance the bridge.

$C_x$  is the unknown capacitor &  $R_x$  is the small leakage resistance of the capacitor

$$\begin{aligned}
 Z_1 &= R_1 \\
 Z_2 &= R_2 \\
 Z_3 &= R_3 \text{ in series with } C_3 \text{ i.e. } R_3 - j/\omega C_3 \\
 Z_4 &= R_x \text{ in series with } C_x \text{ i.e. } R_x - j/\omega C_x
 \end{aligned}$$

$R - jX_C$   
 $R - j \frac{1}{\omega C}$

the condition for balance of the bridge is

$$Z_1 Z_x = Z_2 Z_3$$

$$\text{i.e. } R_1 \left[ R_x - \frac{j}{\omega C_x} \right] = R_2 \left[ R_3 - \frac{j}{\omega C_3} \right]$$

$$R_1 R_x - \frac{j R_1}{\omega C_x} = R_2 R_3 - \frac{j R_2}{\omega C_3}$$

Two complex quantities are equal when both their real & their imaginary terms are equal.

$$\therefore R_1 R_x = R_2 R_3 \quad \& \quad \frac{j R_1}{\omega C_x} = \frac{j R_2}{\omega C_3}$$

$$\therefore \underline{\underline{R_x = \frac{R_2 R_3}{R_1}}}$$


$$\underline{\underline{C_x = \frac{C_3 R_1}{R_2}}}$$

Eg:- A capacitance comparison bridge is used to measure a capacitive impedance at a freq of 2 kHz. The bridge constants at balance are  $C_3 = 100 \mu F$ ,  $R_1 = 10 K\Omega$ ,  $R_2 = 50 K\Omega$ ,  $R_3 = 100 K\Omega$ . Find the equivalent series circuit of the unknown impedance.

$$\text{W.K.T } R_x = \frac{R_2 R_3}{R_1} = \frac{50 \times 10^3 \cdot 100 \times 10^3}{10 \times 10^3} = \underline{\underline{500 K\Omega}}$$
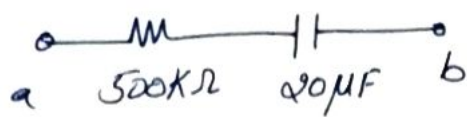
$$\text{Then } C_x = \frac{C_3 R_1}{R_2} = \frac{10 \times 10^3}{50 \times 10^3} \times 100 \times 10^{-6} = \underline{\underline{20 \mu F}}$$






Inductance Comparison bridge — assignment

## Maxwell's Bridge

measures an unknown inductance in terms of a known capacitor. The capacitor is almost a loss-less component.

one arm has a resistance  $R_1$  in parallel with  $C_1$ .
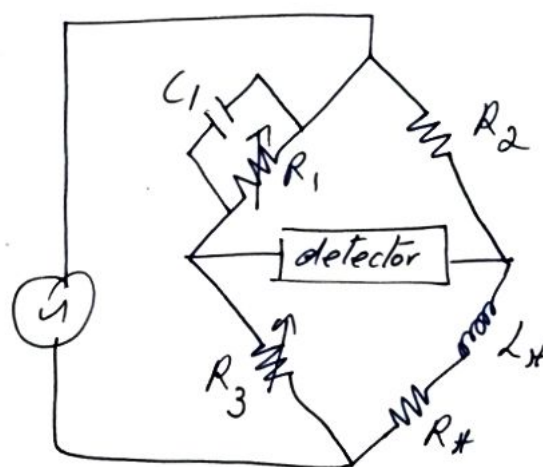
$$\text{W.K.T } Z_1 Z_x = Z_2 Z_3 \rightarrow (1)$$



$$Z_1 = R_1 \text{ in parallel with } C_1 \text{ i.e. } Y_1 = \frac{1}{Z_1}$$

$$= \frac{1}{R_1} + j\omega C_1$$

$$Z_2 = R_2$$

$$Z_3 = R_3$$

$$Z_x = R_x \text{ in series with } L_x \Rightarrow R_x + j\omega L_x$$

Eqn (1) becomes

$$Z_x = Z_2 Z_3 Y_1$$

$$R_x + j\omega L_x = R_2 R_3 \left[ \frac{1}{R_1} + j\omega C_1 \right]$$

$$R_x + j\omega L_x = \frac{R_2 R_3}{R_1} + j\omega C_1 R_2 R_3$$

Equating real terms & imaginary terms

$$\underline{\underline{R_x = \frac{R_2 R_3}{R_1}}} \quad \& \quad j\omega L_x = j\omega C_1 R_2 R_3$$
$$\underline{\underline{i.e. L_x = C_1 R_2 R_3.}}$$

Also.

$$Q = \frac{\omega L_x}{R_x} = \frac{\omega C_1 R_2 R_3 R_1}{R_2 R_3} = \underline{\underline{\omega C_1 R_1.}}$$


Maxwell bridge is limited to the measurement of low Q values (1-10).

This bridge is suited for inductance measurements i.e from 1-1000H. with  $\pm 2\%$  error.

Eg A Maxwell bridge is used to measure an inductive impedance. The bridge constants at balance are  $C_1 = 0.01 \mu F$ ,  $R_1 = 470 k\Omega$ ,  $R_2 = 5.1 k\Omega$  &  $R_3 = 100 k\Omega$ . Find the series equivalent of the unknown impedance.


$$R_x = \frac{R_2 R_3}{R_1} = \frac{100 \times 10^3 \times 5.1 \times 10^3}{470 \times 10^3} = \underline{\underline{1.09 k\Omega}}$$
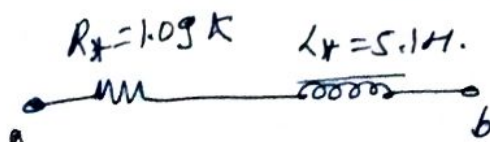
$$L_x = C_1 R_2 R_3 = 0.01 \times 10^{-6} \times 5.1 \times 10^3 \times 100 \times 10^3$$
$$= \underline{\underline{5.1 H}}$$


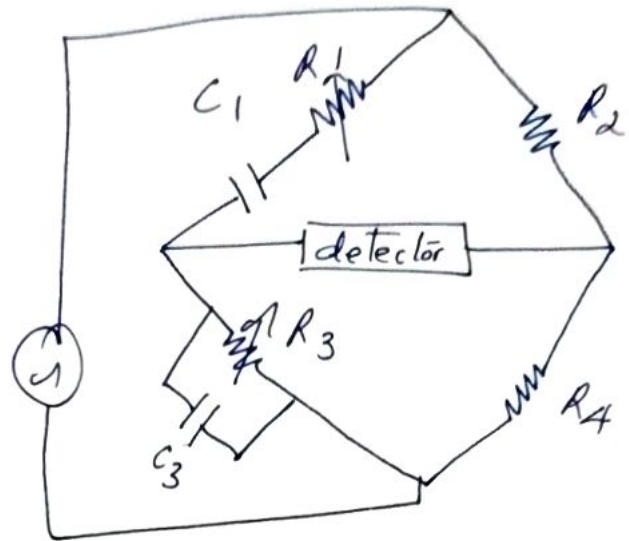
## Wien's Bridge

The Wien bridge has a series RC combination in one arm and a parallel combination in the adjoining arm.



Wien's bridge is used for the measurement of an unknown capacitance with great accuracy. It is ~~used~~ designed to measure freq.

$$Z_1 = R_1 - \frac{j}{\omega C_1}$$

The admittance of the  $\parallel$  arm is

$$Y_3 = \frac{1}{R_3} + j\omega C_3$$

for bridge balance.

$$Z_1 Z_4 = Z_2 Z_3$$

$$\left\{ \left( R_1 - \frac{j}{\omega C_1} \right) R_4 \right\} \left( \frac{1}{R_3} + j\omega C_3 \right) = R_2 R_3$$

$$R_2 = \left( R_1 R_4 - \frac{j R_4}{\omega C_1} \right) \left( \frac{1}{R_3} + j\omega C_3 \right)$$

$$= \frac{R_1 R_4}{R_3} - \frac{j R_4}{\omega C_1 R_3} + R_1 R_4 j\omega C_3 + \frac{\omega C_3 R_4}{\omega C_1}$$



$$R_2 = \frac{R_1 R_4}{R_3} + \frac{C_3 R_4}{C_1} - j \left[ \frac{R_4}{\omega C_1 R_3} - \omega C_3 R_1 R_4 \right]$$

Equating real & imaginary terms

$$R_2 = \frac{R_1 R_4}{R_3} + \frac{C_3 R_4}{C_1} \quad \& \quad \frac{R_4}{\omega C_1 R_3} - \omega C_3 R_1 R_4 = 0$$

$$\frac{R_2}{R_4} = \frac{R_1}{R_3} + \frac{C_3}{C_1} \quad \& \quad \frac{1}{\omega C_1 R_3} = \omega C_3 R_1$$

$\rightarrow \textcircled{A}$

$$\omega^2 = \frac{1}{C_1 C_3 R_1 R_3}$$

$$\omega = \frac{1}{\sqrt{C_1 C_3 R_1 R_3}}$$

w.k.T  $\omega = 2\pi f$ .

$$f = \frac{1}{2\pi \sqrt{C_1 R_1 C_3 R_3}} \quad \textcircled{B}$$

If we satisfy eq  $\textcircled{A}$  & also excite the bridge with the freq of eqn  $\textcircled{B}$  the bridge will be balanced.

In maxt wien bridge C.T.,  $R_1 = R_3 = R$

$$C_1 = C_3 = C.$$

$\therefore$  Eqn A reduces to

$$\frac{R_2}{R_4} = 2. \quad \& \quad \text{Eqn (B) is}$$

$$d = \frac{1}{2\pi RC}.$$

which is the general equation for the freq of the bridge ckt.

Application :-

1) used for measuring freq in the audio range [ 20 - 200 - 2K - 20K Hz ranges ]

2) used for measuring capacitances.

3) used in harmonic distortion analyzer as a notch filter

4) used in Audio freq & Radio freq oscillators as a freq determining element.

Disadvantage :-

Since this is freq sensitive, it is difficult

to balance unless the w/f of the applied  $V_g$  is purely sinusoidal.

eg:- Find the equivalent parallel resistance & capacitance that causes a Wien bridge to null with the following component values.

$$R_1 = 3.1 \text{ k}\Omega \quad R_2 = 25 \text{ k}\Omega \quad R_4 = 100 \text{ k}\Omega$$

$$C_1 = 5.2 \mu\text{F} \quad f = 2.5 \text{ kHz}$$

$$\text{w.k.t } \omega = 2\pi f \\ = 2 \times \pi \times 2.5 \times 10^3 = 15.71 \text{ k rad/s}$$

$$\text{w.k.t } \omega^2 = \frac{1}{C_1 R_1 R_3 C_3}$$

$$C_3 = \frac{1}{\omega^2 C_1 R_1 R_3}$$

$$\text{Sub in } \frac{R_2}{R_4} = \frac{R_1}{R_3} + \frac{C_3}{C_1} \\ = \frac{R_1}{R_3} + \frac{1}{\omega^2 C_1^2 R_1 R_3}$$

$$\frac{R_2}{R_4} = \frac{1}{R_3} \left[ R_1 + \frac{1}{\omega^2 C_1^2 R_1} \right]$$

$$\underline{\underline{R_3 = \frac{R_4}{R_2} \left[ R_1 + \frac{1}{\omega^2 C_1^2 R_1} \right]}}$$



$$R_3 = \underline{\underline{12.4 \text{ K}\Omega}}$$

$$C_3 = \frac{1}{\omega^2 C_1 R_1 R_3}$$

$$= \frac{1}{(15.7 \times 10^3)^2 \times 5.2 \times 10^{-6} \times 3.1 \times 10^3 \times 12.4 \times 10^3}$$


$$= \underline{\underline{20.4 \text{ pF}}}$$

### Problems

i) An ac bridge with terminals A, B, C, D has in AB a pure resistance, Arm BC has a resistance of  $800\Omega$  in parallel with a capacitor of  $0.5\mu\text{F}$ , arm CD has a resistance of  $400\Omega$  in series with a capacitor of  $1.0\mu\text{F}$ . Arm DA has a resistance of  $1000\Omega$ .

i) obtain the value of the frequency for which the bridge can be balanced by first deriving the balance equations connecting the branch impedance.

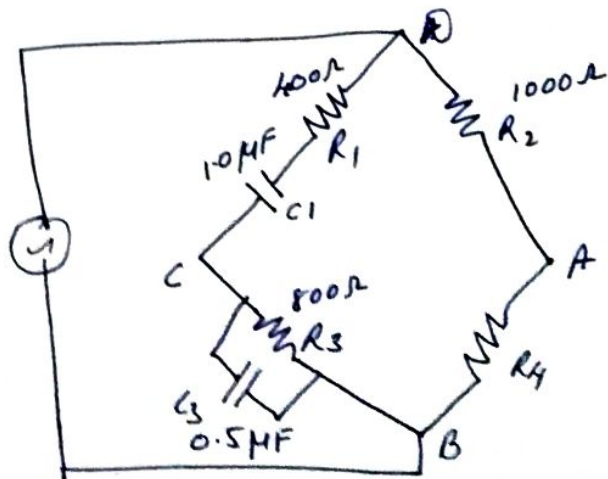ii) calculate the value of the resistance in arm AB to produce balance.



$$i) \quad d = \frac{1}{2\pi \sqrt{C_1 R_1 C_3 R_3}}$$

$$= \frac{1}{2\pi \sqrt{1 \times 10^{-6} \times 400 \times 0.5 \times 10^{-6} \times 800}}$$

$$= \underline{\underline{397.88 \text{ Hz}}}$$

$$ii) \quad R_4 \text{ w.r.t } \frac{R_2}{R_4} = \frac{R_1}{R_3} + \frac{C_3}{C_1}$$

$$R_4 = \frac{R_2}{\left[ \frac{R_1}{R_3} + \frac{C_3}{C_1} \right]} = \frac{1000}{\left[ \frac{400}{800} + \frac{0.5}{1} \right]}$$

$$= \underline{\underline{1000 \Omega}}$$

Q2] The wheatstone bridge is shown in figure. The galvanometer has a current sensitivity of  $12 \text{ mm}/\mu\text{A}$ . The internal resistance of galvanometer is  $200 \Omega$ . Calculate the deflection of the galvanometer caused due to  $5 \Omega$  unbalance in the arm AD.

$$\begin{aligned}
 V_{th} &= I_g \cdot R_{th} \\
 &= 1 \times 10^{-9} \cdot 1000 \\
 &= 1 \mu V.
 \end{aligned}$$

$$\begin{aligned}
 \Delta R &= \frac{V_{th} \times 4R}{F} \\
 &= \frac{1 \times 10^{-6} \times 4 \times 1000}{20}
 \end{aligned}$$

$$\Delta R = 200 \mu \Omega$$

4] The bridge is balanced at  $1000 \text{ Hz}$ . It has following components Arm AB =  $0.2 \mu\text{F}$  pure capacitance  
 Arm BC =  $500 \Omega$  pure resistance, Arm CD =  $300 \Omega$  inductor with  $0.1 \mu\text{F}$ . Find the constants of arm CD, considering it as a series Ckt.


(Maxwell's Ckt)

$$Z_1 = \frac{0-j}{\omega C_1} = 0.2 \mu\text{F}$$

$$Z_2 = R_2 = 500 \Omega$$

$$Z_3 = \frac{1}{\frac{1}{R_3} + j\omega C_3}$$

$$Z_x = R_x + jX_L$$

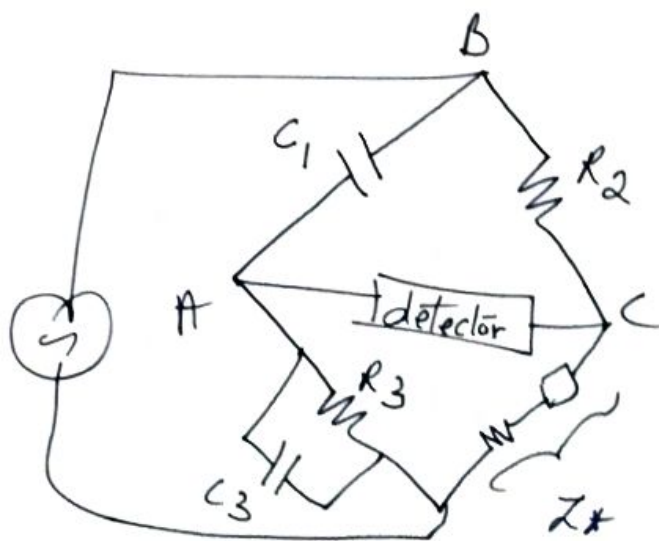



$$Z_1 Z_x = Z_2 Z_3$$

$$Z_x = \frac{Z_2 Z_3}{Z_1} = \frac{Z_2}{Z_1 \gamma_3}$$

$$= \frac{R_2}{-j/\omega C_1 \left[ \frac{1}{R_3} + j\omega C_3 \right]}$$

$$Z_x = \frac{j\omega C_1 R_2}{\frac{1}{R_3} + j\omega C_3}$$

$$= \frac{j 2\pi 1000 \times 0.2 \times 10^{-6} \times 500}{\frac{1}{300} + j 2\pi \times 1000 \times 0.1 \times 10^{-6}}$$

$$= \frac{j 0.6283}{3.3333 \times 10^{-3} + j 6.2831 \times 10^{-4}}$$

$$= \frac{0 + j 0.6283}{3.3333 \times 10^{-3} + j 6.2831 \times 10^{-4}}$$

$$= \frac{0.6283 \angle 90^\circ}{3.388 \times 10^{-3} \angle 10.68^\circ}$$

$\nearrow \text{Re} (0.6283, 90)$   
 $\downarrow$   
 $\text{Re} \tan$

$$= 185.407 \angle 79.32^\circ$$

$$R_x + j\omega L_x = 34.36 + j 182.19 \Omega$$

$$\therefore \underline{R_x = 34.36 \Omega}$$

$$\omega L_x = 182.19$$

$$L_x = \frac{182.19}{2\pi \times 1000}$$

$$= \underline{28.99 \text{ mH}}$$

5] The four arms of a bridge are.

14

Arm ab: an imperfect capacitor  $C_1$  with an equivalent series resistance  $R_1$ .

Arm bc: a non-inductive resistance  $R_3$ .

Arm cd: " " " "  $R_4$

Arm da: an imperfect capacitor  $C_2$  with an equivalent series resistance of  $R_2$  in series with a resistance  $R_2$ .

A supply of  $450\text{Hz}$  is given between terminal a & c & the detector is connected between b & d.  
at balance  $R_2 = 4.8\Omega$ ,  $R_3 = 200\Omega$ ,  $R_4 = 2850\Omega$   
 $C_2 = 0.5\mu\text{F}$ ,  $R_2 = 0.4\Omega$ . calculate the value of  $R_1$   
&  $C_1$  & also the dissipating factor of this capacitor.


$$Z_1 Z_4 = Z_3 Z_2$$

$$(R_1 - j/\omega C_1) R_4 = R_3 (R_2 + R_2 - j/\omega C_2)$$

$$R_1 R_4 - \frac{j R_4}{\omega C_1} = R_2 R_3 + R_2 R_3 - \frac{j R_3}{\omega C_2}$$

$$R_1 = \frac{R_2 R_3 + R_2 R_3}{R_4} = \frac{4.8(200) + 0.4(200)}{2850}$$
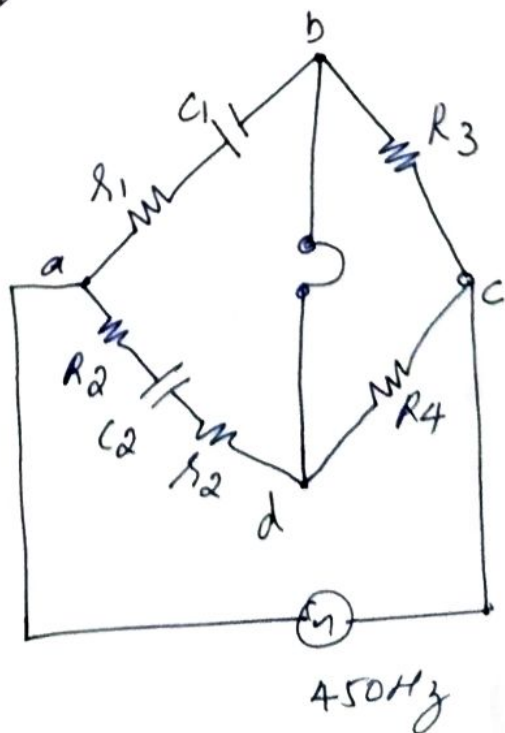
$$= \underline{\underline{0.3649\Omega}}$$



$$\frac{R_4}{C_1} = \frac{R_3}{C_2}$$

$$C_1 = \frac{R_4 C_2}{R_3} = \frac{2850 (0.5 \times 10^{-6})}{200} = \underline{\underline{7.125 \mu F}}$$

$$\begin{aligned} \text{dissipating factor} &= \omega C_1 r_1 \\ &= 2\pi (450) \times 7.125 \times 10^{-6} \times 0.3649 \\ &= \underline{\underline{7.35 \times 10^{-3}}} \\ &= \underline{\underline{0.00735}} \end{aligned}$$