

No matter how perfect the system design, the application of a load to a two-port system will affect the voltage gain. Therefore, there is no possibility of a situation where A_{v1} , A_{v2} , and so on, of Fig. 5.69 are simply the no-load values. The loading of each succeeding stage must be considered. The no-load parameters can be used to determine the loaded gains of Fig. 5.69, but Eq. (5.93) requires the loaded values.

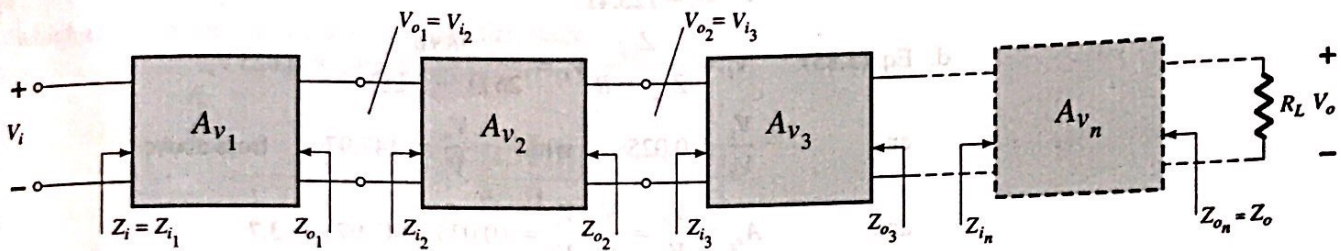


FIG. 5.69
Cascaded system.

EXAMPLE 5.14 The two-stage system of Fig. 5.70 employs a transistor emitter-follower configuration prior to a common-base configuration to ensure that the maximum percentage of the applied signal appears at the input terminals of the common-base amplifier. In Fig. 5.70, the no-load values are provided for each system, with the exception of Z_i and Z_o for the emitter-follower, which are the loaded values. For the configuration of Fig. 5.70, determine:

- The loaded gain for each stage.
- The total gain for the system, A_v and A_{v_r} .
- The total current gain for the system.
- The total gain for the system if the emitter-follower configuration were removed.

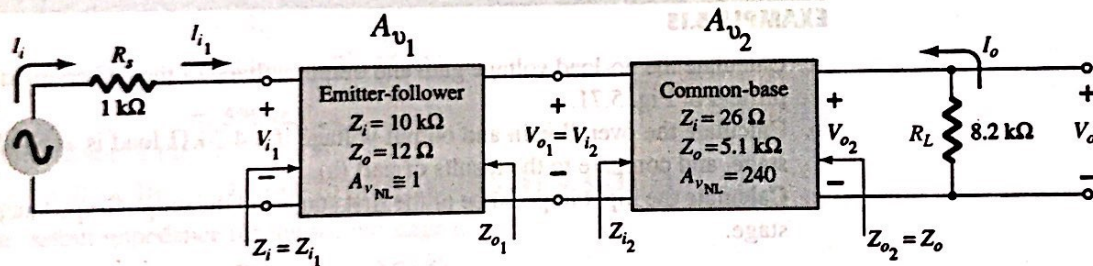


FIG. 5.70
Example 5.14.

Solution:

- For the emitter-follower configuration, the loaded gain is (by Eq. (5.88))

$$V_{o1} = \frac{Z_{i2}}{Z_{i2} + Z_{o1}} A_{v_{NL}} V_{i1} = \frac{26 \Omega}{26 \Omega + 12 \Omega} (1) V_{i1} = 0.684 V_{i1}$$

and $A_{v1} = \frac{V_{o1}}{V_{i1}} = 0.684$

For the common-base configuration,

$$V_{o2} = \frac{R_L}{R_L + R_{o2}} A_{v_{NL}} V_{i2} = \frac{8.2 \text{ k}\Omega}{8.2 \text{ k}\Omega + 5.1 \text{ k}\Omega} (240) V_{i2} = 147.97 V_{i2}$$

and $A_{v2} = \frac{V_{o2}}{V_{i2}} = 147.97$

- Eq. (5.93): $A_{v_r} = A_{v1} A_{v2}$
 $= (0.684)(147.97)$
 $= 101.20$